

54000
1000

53000

Diode + Transistors → Discrete Components

Putting few diode + transistors - small scale integration

6 Introduction to micro-computer and micro-computer organisation.

Types of logic circuits

1. Combinational logic circuits.
2. Sequential logic circuits.

Combinational logic circuits <memoryless>

- Depends on input only <no memory>

ex > output depend on input only >

Adders, encoders, decoders, multiplexers, demultiplexers
comparators - - -

Sequential logic circuits

- Circuits which have input set, logic network, output and memory - main part

// Given input, it looks on input and checks previous output and decide the current output //

- > Present output depends not only present input but also the previous output.

example of S.L.C

1. Latches

2. Flip flops (basic building block of all memory devices)

Unit 9

$1+1=2$
 $1+1=10$
 $5+5=10$

Combinational logic circuits

Types:

1. Binary adder.

- Most basic arithmetic operation is addition of 2 binary digits

- It consists of 4 elementary operations

$$0+0=0$$

$$0+1=1$$

$$1+0=1$$

$$1+1=10$$

carry

Half-adder.


- It performs addition of 2 bits which can be arranged in a truth table.


A	B	C	S	C = carry	S = sum
0	0	0	0		
0	1	0	1	$\bar{A}B$	
1	0	0	1	$A\bar{B}$	
1	1	1	0		

Boolean expression for sum and carry.

$$\text{Sum} = \bar{A}B + A\bar{B} \quad \text{or} \quad S = \bar{A}B + A\bar{B}$$
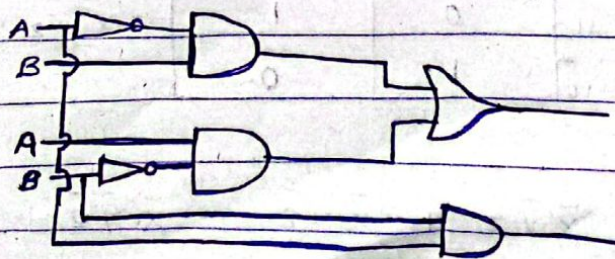
$$\text{Carry} = AB \quad \text{or} \quad C = AB$$



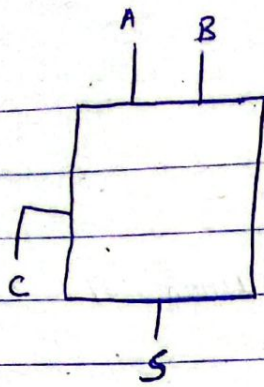

x	y	z	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

// when you hv more than one ~~add~~ binary numbers, half adder sees it difficult

use K-map of Sum.

3 inputs = $2^3 = 8$ cells.

		z	
xy		0	1
$\bar{x}\bar{y}\bar{z}$	00	0	1
	01	1	0
$x\bar{y}\bar{z}$	11	0	1
	10	1	0

$$S = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy z$$

2


K-map for Carry.

X\Y	2	0	1
00	0	0	0
01	0	0	1
11	1	1	1
10	0	1	1

Handwritten annotations:
- A red circle around the '1' at (01, 1) is labeled xyz .
- A red circle around the '1' at (11, 1) is labeled xz .
- A red circle around the '1' at (10, 1) is labeled xz .
- A red circle around the '1' at (11, 0) is labeled xy .


$$C = yz + xz + xy$$

logic circuit for carry.


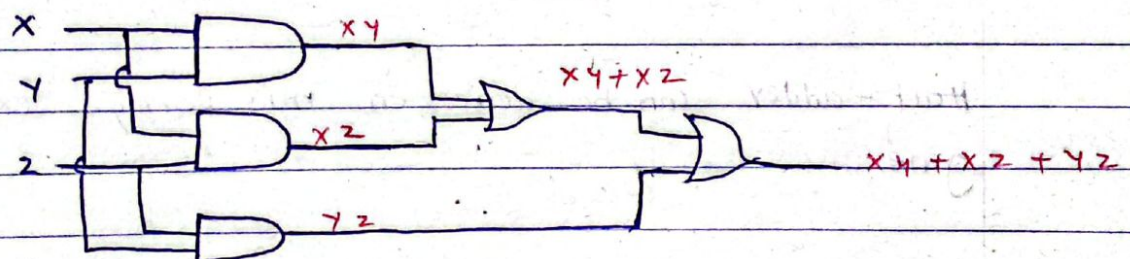


logic circuit for Sum.
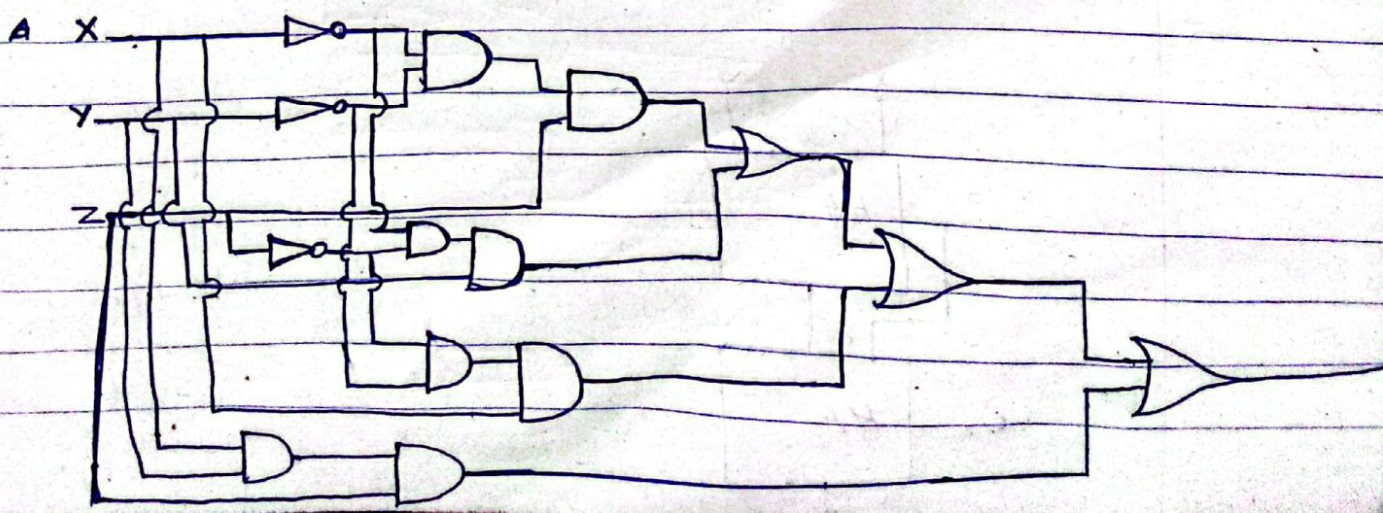
$$S = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xyz$$



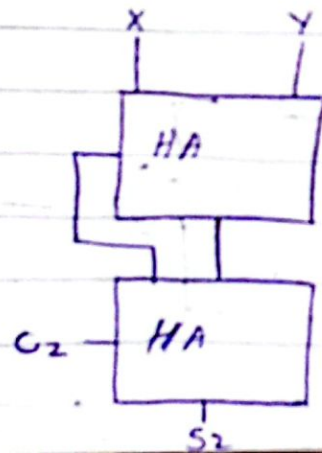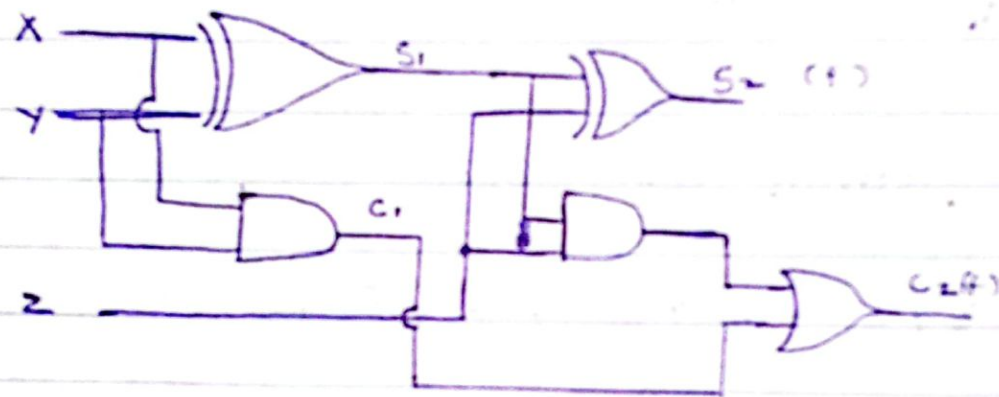Half-adder can be done in this using exclusive or gate



Digital circuits to implement

$$21_{10} + 11_{10} =$$

$$2 \overline{) 21}$$

$$2 \overline{) 10} - 1$$

$$2 \overline{) 5} - 0$$

$$2 \overline{) 2} - 1$$

$$2 \overline{) 1} - 0 = 10101$$

$$6 - 1$$

$$2 \overline{) 11}$$

$$2 \overline{) 5} - 1$$

$$2 \overline{) 2} - 1$$

$$2 \overline{) 1} - 0$$

$$1$$

= 1011 making each 4 bit add 01011


Using four bit

$$A = A_3 A_2 A_1 A_0$$


$$B = B_3 B_2 B_1 B_0$$

} A + B
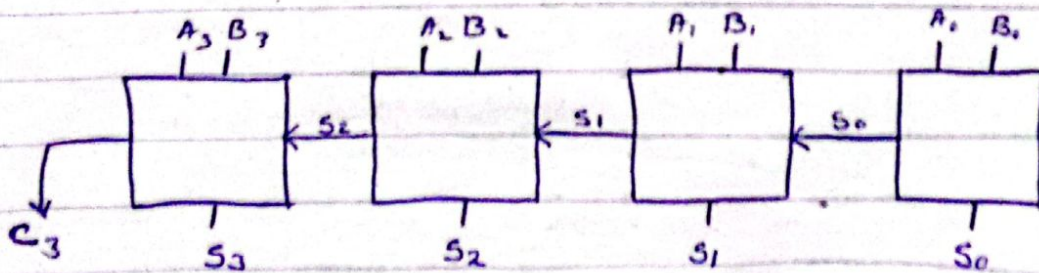
$$A + B = (A_0 + B_0) (A_1 + B_1) (A_2 + B_2) (A_3 + B_3)$$



ALU
BCD

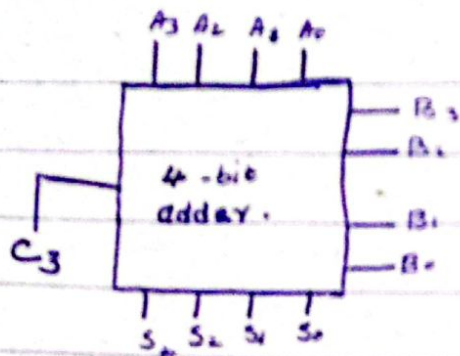

- An ~~n-bit~~ ^{n-bit} ~~full~~ adder requires ^{full} n adders with each output carry connected to input carry of next higher-order full adder.