

CSC 211: DIGITAL ELECTRONICS II

- **MEDIUM SCALE INTEGRATED (MSI) DEVICES**

Dr. Ronoh Saweh
Department of Computer Science
KIBABII UNIVERSITY

INTRODUCTION

- There are several specialized MSI components that have extensive use in digital systems. These are classified as standard components.
- *These include adders, subtractors, comparators, decoders, encoders and multiplexers.*

Binary Adder–Subtractor

- The most basic arithmetic operation is the addition of two binary digits. This simple addition consists of four possible elementary operations:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

Binary Adder–Subtractor

- The first three operations produce a sum (S) of one digit, but when both augend and addend bits are equal to 1 a carry (C) is also generated (this propagates to the next most significant stage of the addition).

Half Adder


- Performs the addition of two bits.

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy'$$

$$C = xy$$


- Implementation**

 

$$S = x'y + xy'$$

$$C = xy$$

Half Adder

 

$$S = x \oplus y$$

$$C = xy$$

Full Adder

- Performs the arithmetic sum of three bits

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full Adder



		yz		y	
		00	01	11	10
x	0		1		1
x	1	1		1	
				z	

$$S = x'y'z + x'yz' + xy'z' + xyz$$

		yz		y	
		00	01	11	10
x	0			1	
x	1		1	1	1
				z	


$$C = xy + xz + yz$$

$$= xy + xy'z + x'yz$$

  

Alternative Implementation

 - The full adder can also be realized with two half adders and one OR-gate:



- The output S from the second half adder is the X OR of z and the output of the first half adder, giving:

$$\begin{aligned} S &= z \oplus (x \oplus y) \\ &= z'(xy' + x'y) + z(xy' + x'y')' \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= xy'z' + x'yz' + xyz + x'y'z \end{aligned}$$

- The carry output is:


$$C = z(xy' + x'y) + xy = xy'z + x'yz + xy$$

Binary Adder

Binary Adder

- Produces the arithmetic sum of two binary numbers.
- It can be realized with full adders (FAs) connected in cascade.
- A 4-bit binary ripple adder is realized as shown below:

Binary Adder

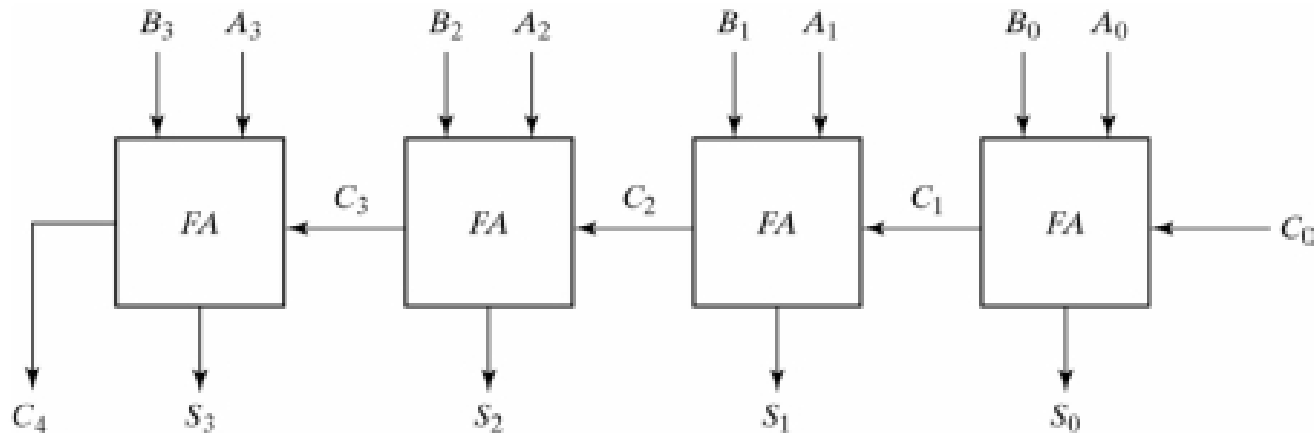

- An n-bit adder requires n full adders with each output carry connected to the input carry of the next higher-order full adder.

Example


- Consider the two binary numbers, $A = 1011$ and $B = 0011$.
- Their sum $S = 1110$ is formed with the 4-bit adders as follows:

<i>Subscript i:</i>	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Carry Propagation

- The longest propagation time in a binary ripple adder is the time it takes the carry to propagate through all full adders.
- The number of gate levels for the carry propagation can be found from the circuit of the full adder:

Carry Propagation

 

Carry Propagation


- The subscript i denotes a given stage in the adder.
- The signals P_i and G_i settle to their steady state values after they propagate through their gates.
- P_i and G_i are common to all full adders and depend only on the input augend and addend bits.

Carry Propagation

- The signal from the input carry C_i to the output carry C_{i+1} , propagates through two gates.
- If there are four full adders, the output carry C_4 would have $2 \times 4 = 8$ gate levels from C_0 to C_4 .
- Clearly, carry propagation time the limiting factor on the speed with which two numbers are added.

Carry Propagation

 - The most widely used technique for reducing the carry propagation time in a parallel adder employs the principle of carry lookahead. Consider again the circuit of the full adder:



Carry Propagation

- If two new binary variables are defined:

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

- the output sum and carry can be expressed as:

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

Carry Propagation

- G_i is called a carry generate and it produces a carry of 1, regardless of the input carry C_i .
- P_i is called a carry propagate because it is the term associated with the propagation of the carry from C_i to C_{i+1} .
- We can now write the Boolean functions for the carry outputs of each stage and substitute for each C_i its value from the previous equations

Carry Propagation

C_0 = input carry


$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

- These expressions are implemented in the following carry lookahead generator:


Carry Propagation

 

Carry Propagation

- The construction of a 4-bit adder with a carry lookahead scheme is shown below:
- All output carries are generated after a delay through two levels of gates. Thus outputs S_1 through S_3 have equal propagation times. The two level circuit for the output carry C_4 is not shown. This can be derived by the equation-substitution method.


Carry Propagation

 

Binary Subtractor

- The subtraction of unsigned binary numbers can be simplified by means of complements.
- For example, $A - B$ can be done by taking the 2's complement of B and adding it to A .
- The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits.
- The 1's complement can be realized with inverters and a 1 can be added to the sum through the input carry.
- A 4-bit adder-subtractor circuit is shown below:

Binary Subtractor

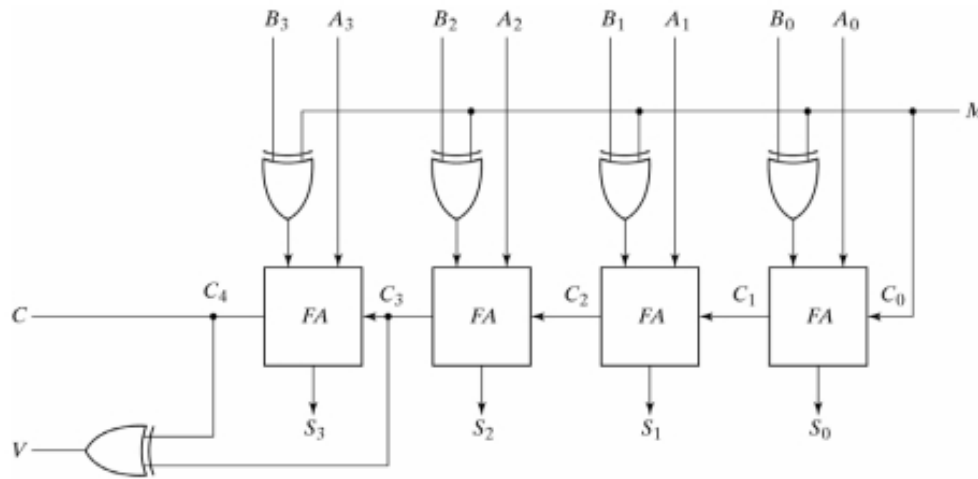

- $M = 0$; addition, $M = 1$; subtraction
- The V bit detects an overflow when the two binary numbers to be added are signed.

Overflow

- Sometimes, when an adder/subtractor is using signed arithmetic, there is arithmetic overflow from the most significant magnitude bit into the sign bit.
- An overflow may occur if the two numbers added are both positive or negative.
- An example of 4 possible situations that may arise is given below for a 4-bit ($n = 4$) word.
- For each case the carries C_{n-1} and C_n are recorded:

Overflow

	$C_n C_{n-1}$		$C_n C_{n-1}$	
	0 0		0 1	→ interpreted as -5
+1	<u>0,001</u>	+5	<u>0,101</u>	
+3	<u>0,011</u>	+6	<u>0,110</u>	
+4	0,100	+11	<u>1,011</u>	

	$C_n C_{n-1}$		$C_n C_{n-1}$	
	1 1		1 0	→ interpreted as +5
+5	<u>0,101</u>	-5	<u>1,011</u>	
-3	<u>1,101</u>	-6	<u>1,010</u>	
+2	0,010	-11	<u>0,101</u>	

Overflow

- In the case where the sum should +11 or -11, the corresponding binary sum is wrong.
- It is obvious that an overflow flag should be raised when $C_{n-1} = 1$ and $C_n = 0$, or, when $C_{n-1} = 0$ and $C_n = 1$.
- Hence, the equation for overflow is:

$$V = C_{n-1} \oplus C_n$$


Decimal Adder

- Computers or calculators that perform arithmetic operations directly in the decimal number system represent decimal numbers in binary-coded form.
- The 8421 weighted coding scheme is the most commonly occurring in digital systems and is often referred to as simply BCD (binary-coded decimal).

Decimal Adder

- When using BCD, a single-decade decimal adder can be realized by first performing conventional binary addition on two binary-coded operands and then applying a corrective procedure.
- This is illustrated below:

Decimal Adder

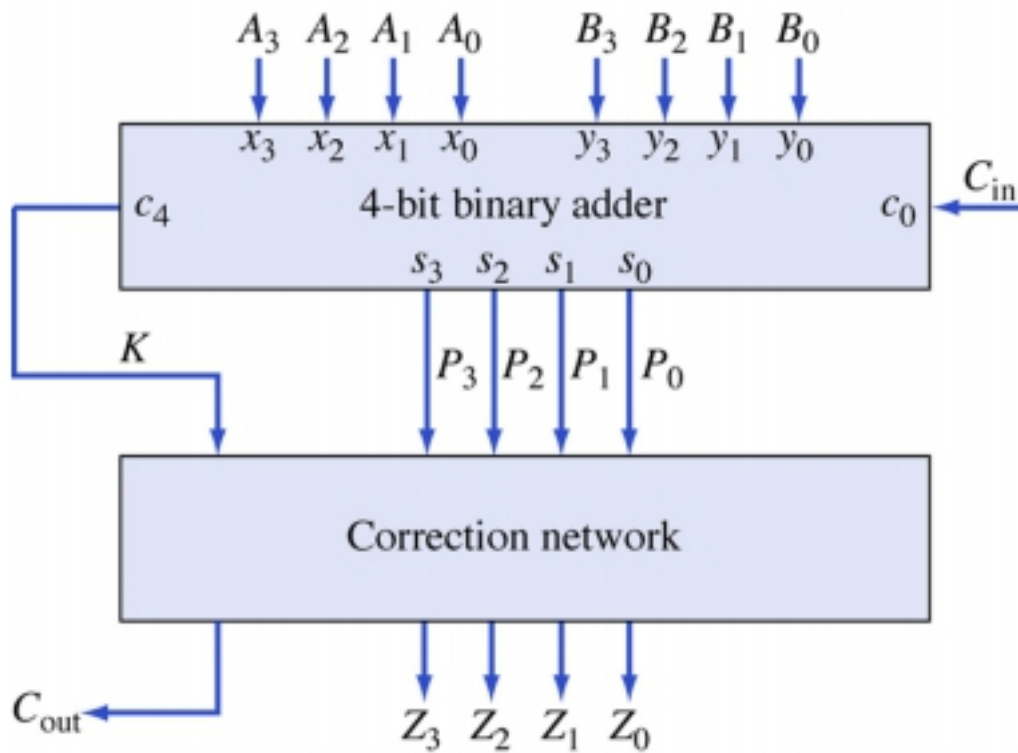

Decimal Adder

Decimal sum	Binary sum					Required BCD sum				
	K	P_3	P_2	P_1	P_0	C_{out}	Z_3	Z_2	Z_1	Z_0
0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0	0	0	1
2	0	0	0	1	0	0	0	0	1	0
3	0	0	0	1	1	0	0	0	1	1
4	0	0	1	0	0	0	0	1	0	0
5	0	0	1	0	1	0	0	1	0	1
6	0	0	1	1	0	0	0	1	1	0
7	0	0	1	1	1	0	0	1	1	1
8	0	1	0	0	0	0	1	0	0	0
9	0	1	0	0	1	0	1	0	0	1
10	0	1	0	1	0	1	0	0	0	0
11	0	1	0	1	1	1	0	0	0	1
12	0	1	1	0	0	1	0	0	1	0
13	0	1	1	0	1	1	0	0	1	1
14	0	1	1	1	0	1	0	1	0	0
15	0	1	1	1	1	1	0	1	0	1
16	1	0	0	0	0	1	0	1	1	0
17	1	0	0	0	1	1	0	1	1	1
18	1	0	0	1	0	1	1	0	0	0
19	1	0	0	1	1	1	1	0	0	1

Decimal Adder

- No correction to the binary sum is needed when
- $KP_3P_2P_1P_0 \leq 01001$.
- However, 0110 (decimal 6) must be added to
- $P_3P_2P_1P_0$ when $KP_3P_2P_1P_0 > 01001$.
- The logic circuit that detects the necessary correction can be derived from the table entries.
- Clearly, a correction is needed when the binary sum has an output carry $K = 1$.
- For the other six combinations from 1010 through 1111 (that also need a correction), a Boolean expression is required to detect them:

Decimal Adder

		P_1P_0			
		00	01	11	10
P_3P_2	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	0	0	1	1

$$f = P_3P_2 + P_3P_1$$


Decimal Adder

- The condition for a correction and an output carry can be expressed by the Boolean function:

$$\text{Add 6} = K + P_3P_2 + P_3P_1$$

- The logic diagram of a single-decade BCD adder is shown below:

Decimal Adder

 

Decimal Adder

- Whenever $C_{out} = 0$, the outputs from the upper 4-bit binary adder are sent to the lower 4-bit adder and decimal 0 is added.
- However, whenever $C_{out} = 1$, decimal 6 is added to the outputs of the upper 4-bit binary adder so that the correct sum digit is obtained.
- A decimal adder for two n-digit BCD numbers can be constructed by cascading the above system in much the same way as was done for the ripple binary adder.