8254 Programmable Timer

A diagram of Intel's 8254 interval timer/event counter is given in Figure 4.5. The 8254 consists of three identical counting circuits, each of which has CLK and GATE inputs and an OUT output. Each can be viewed as containing a Control and Status Register pair, a Counter Register (CR) for receiving the initial count, a Counter Element CCE) which performs the counting but is not directly accessible from the processor, and an Output Latch (OL) for latching the contents of the CE so that they can be read. The CR, CE, and OL are treated as pairs of 8-bit registers. (Physically, the registers are not exactly as depicted, but to the programmer the figure is conceptually accurate.)

The registers can be accessed according to the following table:

CS	RD	WR	A 1	AO	Transfer
0	1	0	0	0	To counter 0 CR
0	1	0	0	1	To counter 1 CR
0	1	0	1	0	To counter 2 CR
0	1	0	1	1	To a control register or indicates a command
0	0	1	0	0	From counter 0 OL or status register
0	0	1	0	1	From counter 1 OL or status register
0	0	1	1	0	From counter 2 OL or status register

 


Figure 4.5: Diagram of the 8254

where 0 means low and 1 means high. All other combinations result in the data pins being put into their high-impedance state. When A1 =AO= 1, whether a control register is being written into or a command is being given depends on the MSBs of the byte being output. For the last three combinations, whether an OL or status register is read is determined by a previous command.

There are two types of commands, the counter latch command, which causes the CE in the counter specified by the two MSBs of the command to be latched into the corresponding OL, and the read back

command, which may cause a combination of the CEs to be latched or "prepare" a combination of status registers to be read. To prepare a status register means to cause it to be read the next time a read operation inputs from the counter. When the two MSBs are 00, 01, or 10 a counter latch command is indicated, but if they are 11 a read back is to be performed. In a latch command bits 5 and 4 must be 0 and the remaining bits are unused. The read back command has the format:

		COUNT	CTAT	CNITO	CNITA	CNITO	^
1	1	COONT	SIAI	CN12	CNII	CNIO	U

If the COUNT bit is 0, then the CEs for all of the counters whose CNT bits are 1 are latched. If CNTO=CNT2=1 but CNT1=0, then the CEs in counters 0 and 2 are latched but the CE in counter 1 is not latched. Similarly, STAT=0 causes the counters' status registers to be prepared for input. CEs can be latched and status registers can be prepared in the same command.

The formats of the control and status registers are given in Figure 4.6. If the two MSBs of an output are both 1, they indicate that the output is to be a read back command; otherwise, they specify a counter. If they specify a counter and bits 4 and 5 are both 0, then a latch command is indicated and it is directed to the control register of the counter specified by the top 2 bits, but if they are not both 0, then they indicate the type of the input from OL or output to CR. The combination 01 indicates that the Read/Write operations are from/to the OL_L/CR_L, 10 indicates that they are from/to the OL_M /CR_M, and 11 indicates that these operations are to occur in pairs, with the first byte coming from/going to OL_L/CR_L and the second from/to OL_M/CR_M. A 1-byte write to CR will cause the other byte to be zeroed. Bits 1, 2, and 3 determine the mode and bit 0 specifies the format of the count. Given that N is the initial count, the modes are:

 


Figure 4.6: Control and status registers for 8254 counters

Mode 0 (Interrupt on Terminal Count)—GATE = 1 enables counting and GATE = 0 disables counting, and GATE has no effect on OUT. The contents of CR are transferred to CE on the first CLK pulse after CR is written into by the processor, regardless of the signal on the GATE pin. The pulse that loads CE is not included in the count. OUT goes low when there is an output to the control register and remains low until the count goes to 0. Mode 0 is primarily for event counting.

Mode 1 (Hardware Retriggerabic One-Shot) —After CR has been loaded with N, a 0-to-1 transition on GATE will cause CE to be loaded, a 1-to-0 transition at OUT, and the count to begin. When the count reaches 0 OUT will go high, thus producing a negative-going OUT pulse N clock periods long.

Mode 2 (Periodic Interval Timer) —After loading CR with N, a transfer is made from CR to CE on the next clock pulse. OUT goes from 1 to 0 when the count becomes 1 and remains low for one CLK pulse; then it returns to 1 and CE is reloaded from CR, thus giving a negative pulse at OUT after every N clock cycles. GATE = 1 enables the count and GATE=0 disables the count. A 0-to-1 transition on GATE also causes the count to be reinitialized on the next clock pulse. This mode is used to provide a programmable periodic interval timer.

Mode 3 (Square-Wave Generator) —It is similar to mode 2 except that OUT goes low when half the initial count is reached and remains low until the count becomes 0. Hence the duty cycle is changed. As before, GATE enables and disables the count and a 0-to-1 transition on GATE reinitializes the count. This mode may be used for baud rate generation.

Mode 4 (Software-Triggered Strobe)—It is similar to mode 0 except that OUT is high while the counting is taking place and produces a one-clock-period negative pulse when the count reaches 0.

Mode 5 (Hardware-Triggered Strobe—Retriggerabic)—After CR is loaded, a O-to-I transition on GATE will cause a transfer from CR to CE during the next CLK pulse. OUT will be high during the counting but will go low for one CLK period when the count becomes 0. GATE can reinitialize counting at any time.

For all modes, if the initial count is 0, it will be interpreted as 2^{16} or 10^4 depending on the format of the count. The above descriptions were only to provide an overall idea of the operation of the 8254 in the various modes.